
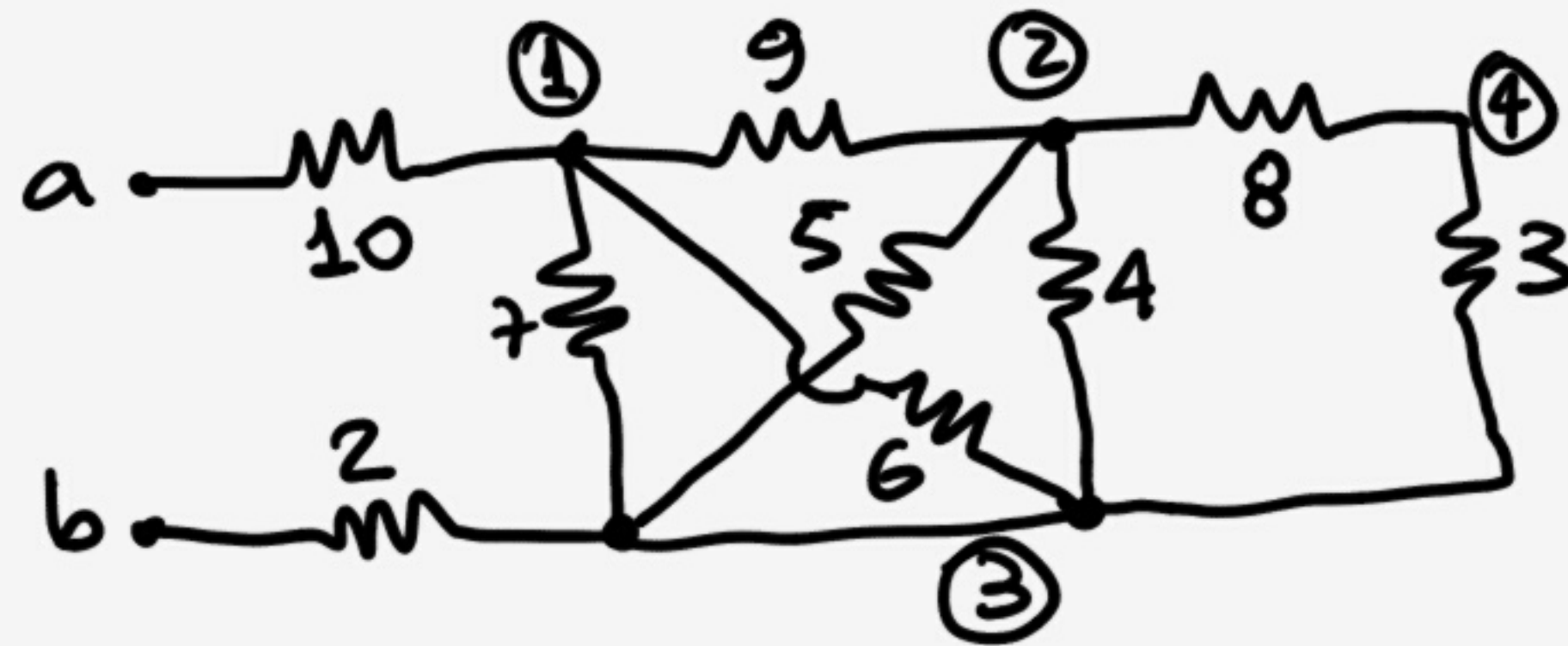


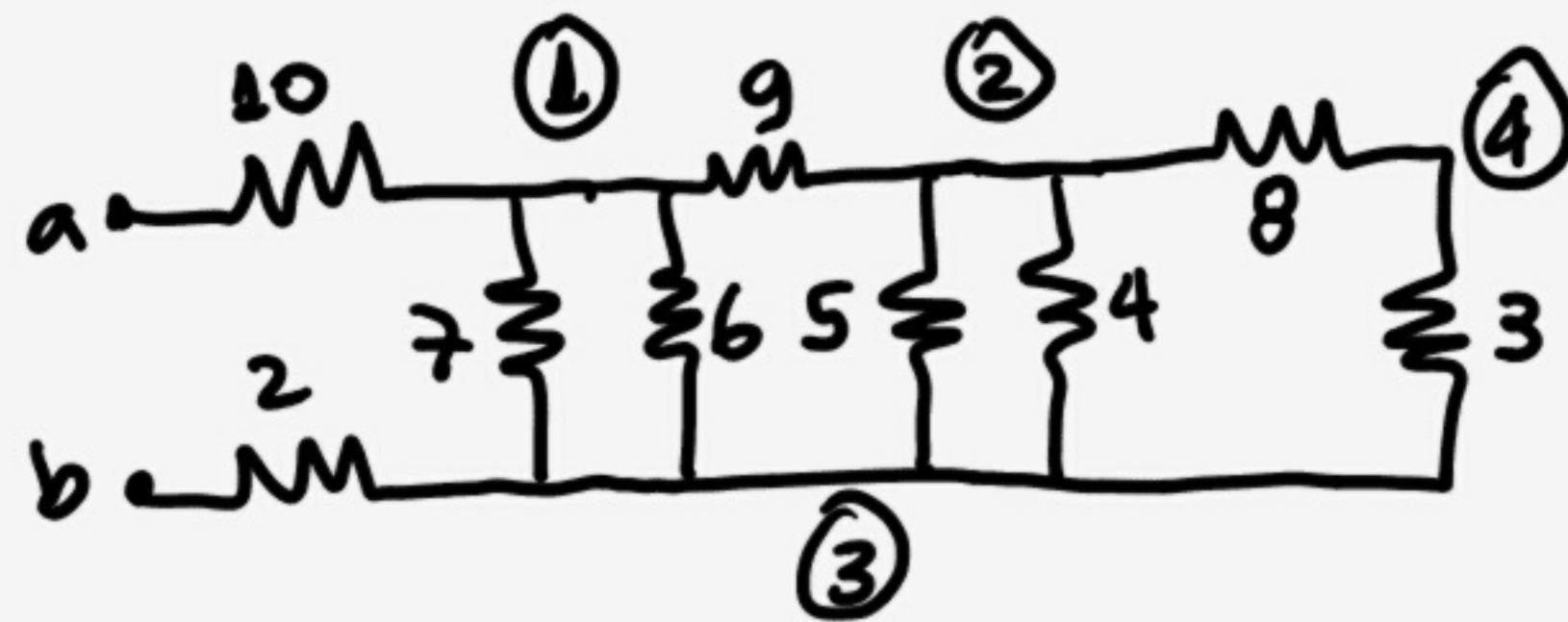
Encontrar la resistencia equivalente R_{ab} :



Solución:

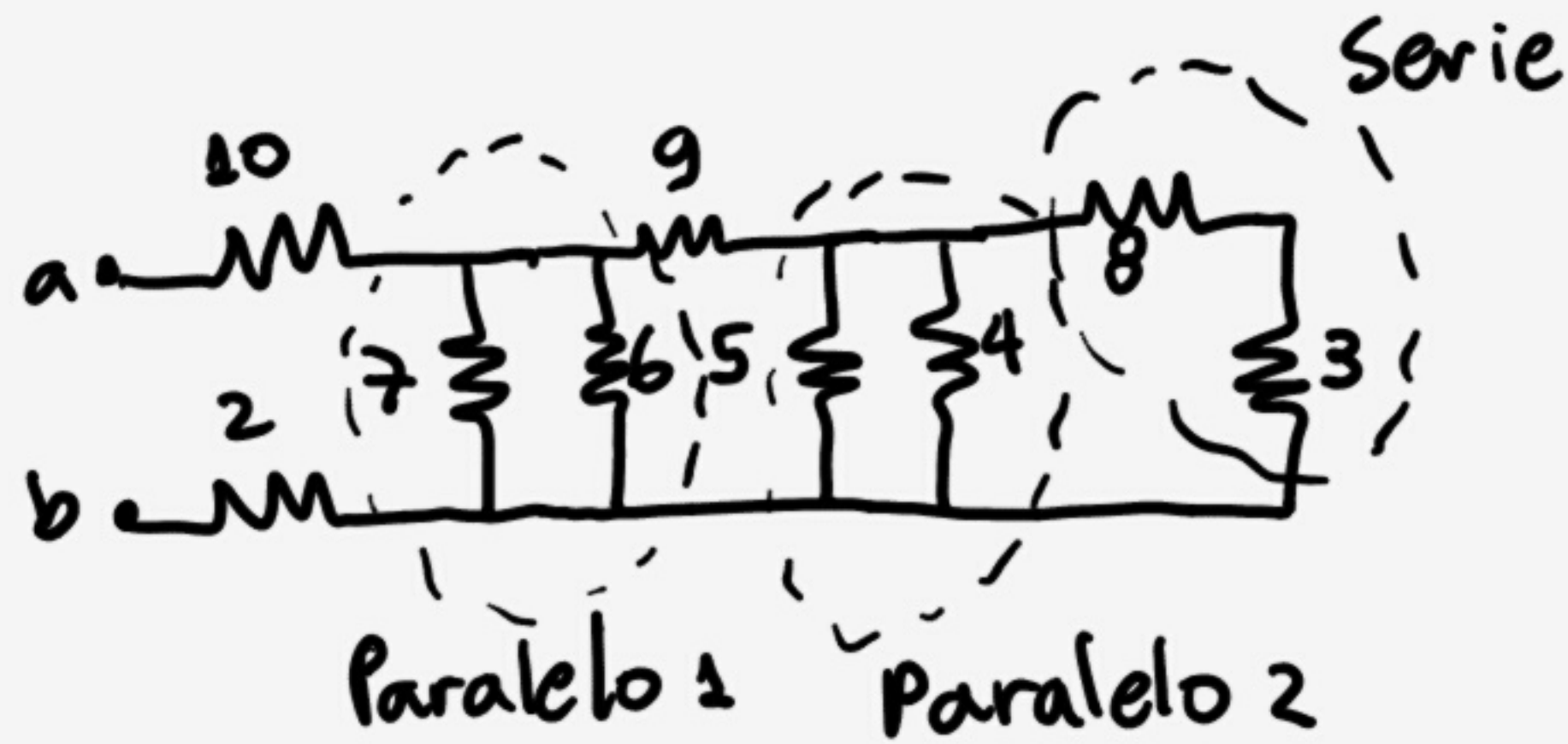Presentando el circuito de otra manera para facilitar su análisis:






Serie: $8 + 3 = 11$

Paralelo 1: $\frac{7 \times 6}{7 + 6} = \frac{42}{13}$

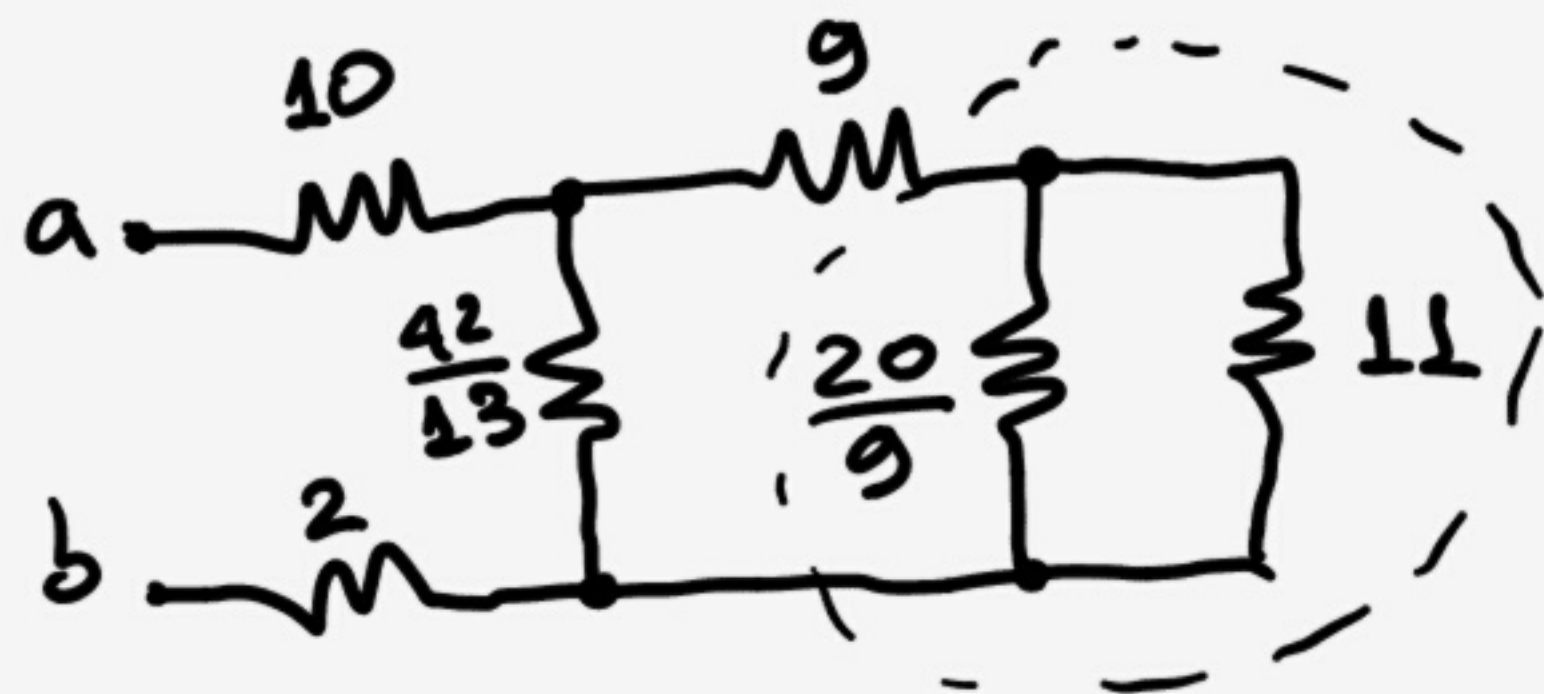Paralelo 2: $\frac{5 \times 4}{5 + 4} = \frac{20}{9}$



Paralelo: $\frac{\frac{20}{9} \times 11}{\frac{20}{9} + 11} = \frac{\frac{220}{9}}{\frac{119}{9}} = \frac{220}{119}$



Serie: $\frac{220}{119} + 9 = \frac{1291}{119}$



Paralelo:

$$\frac{\frac{42}{13} \times \frac{129}{19}}{\frac{42}{13} + \frac{129}{19}} = 2,5$$



Serie: $10 + 2,5 + 2 = 14,5$



