

Taller de fasores e impedancia:

1) Evalúe los siguientes números complejos:


$$a) \frac{10 \angle 30^\circ + (3 - j4)}{(2 + j4)(3 - j5)^*}$$

$$R: / 0,565 \angle -41,03^\circ$$

$$b) [(5 + j2)(-1 + j4) - 5 \angle 60^\circ]^*$$


$$R: / -15,5 + j13,67$$

2) Encuentre $v(t)$ e $i(t)$:

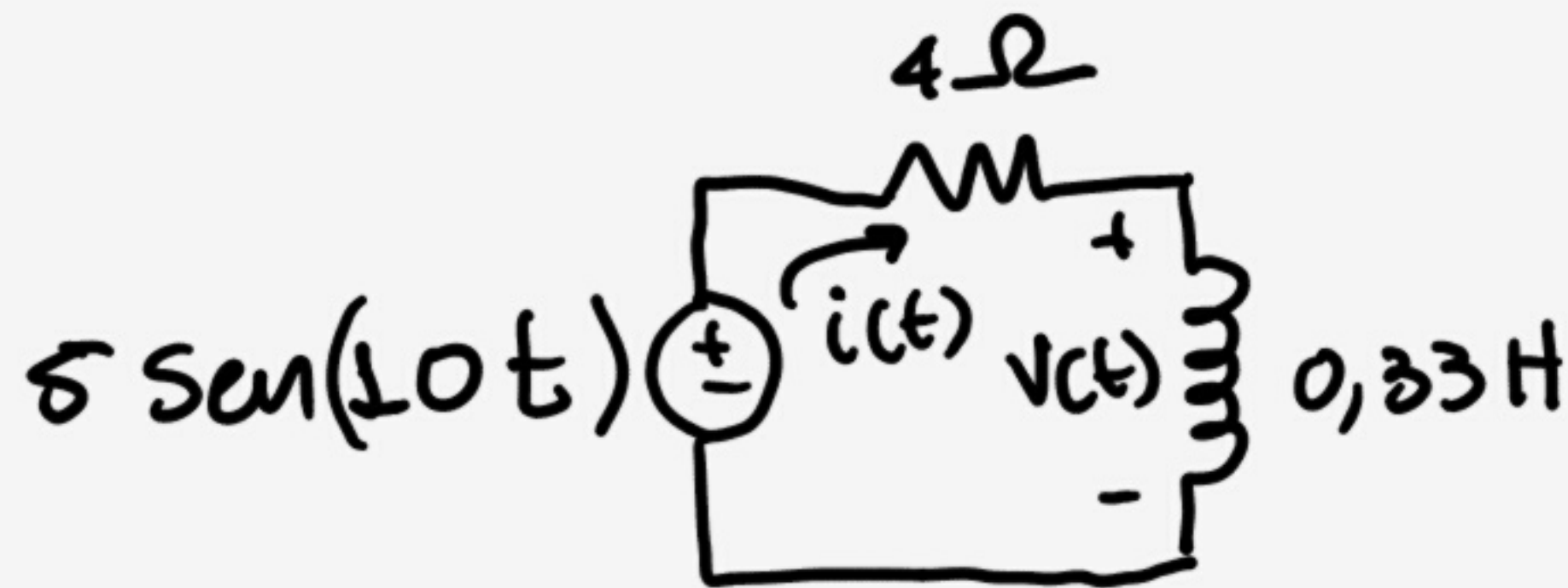


3) Encontrar $i(t)$:

a)

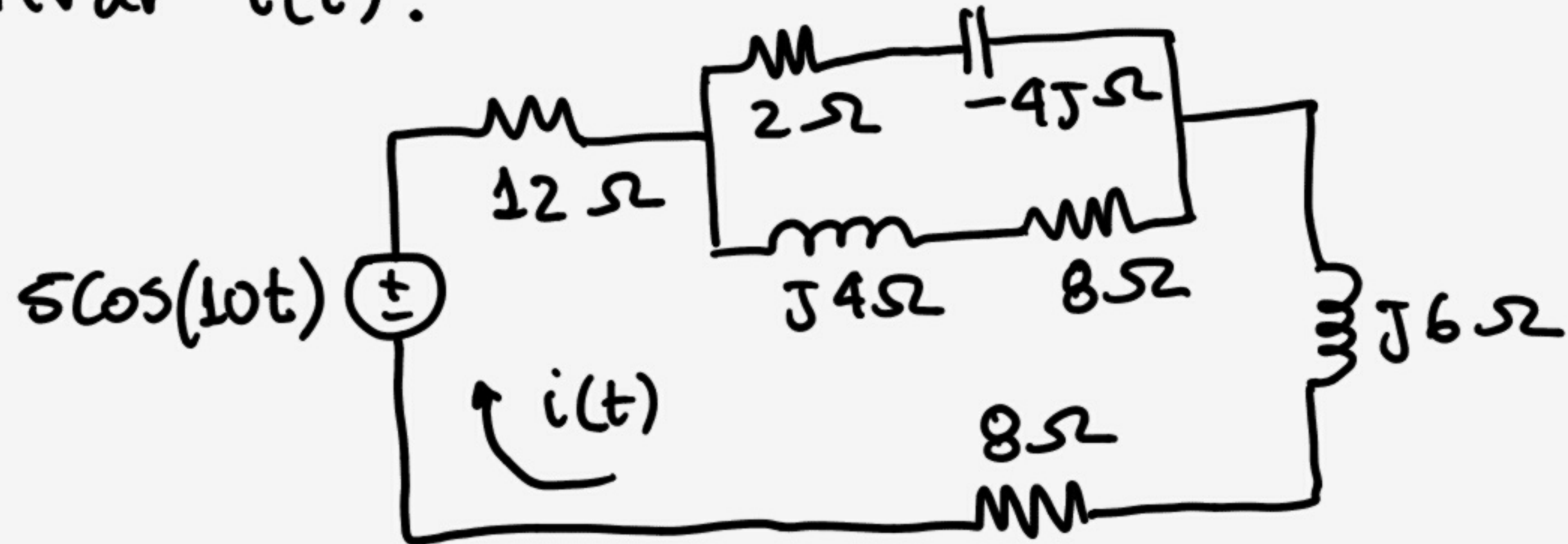


b)

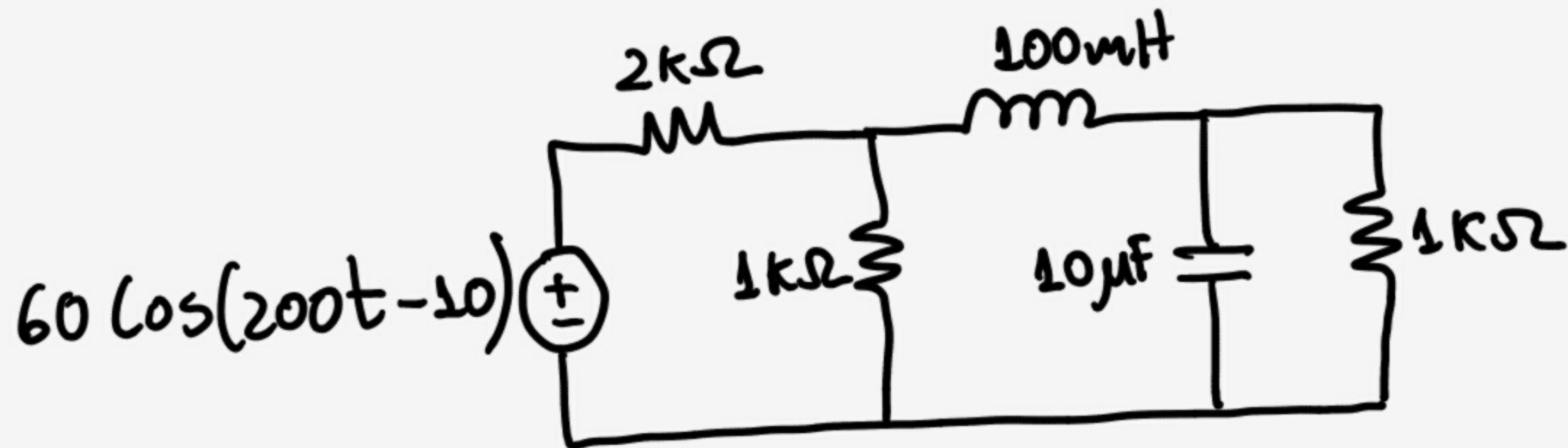


4) Halle $i(t)$ y $v(t)$ en cada uno de los circuitos.


a)

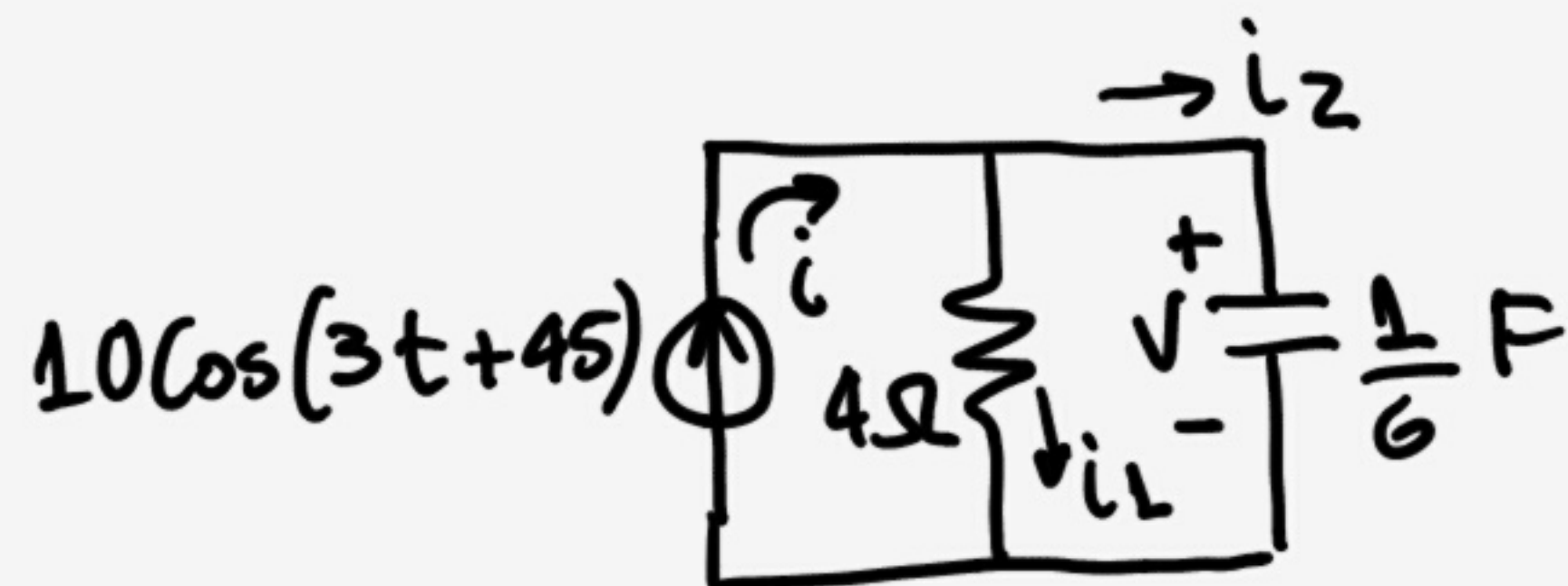


b)

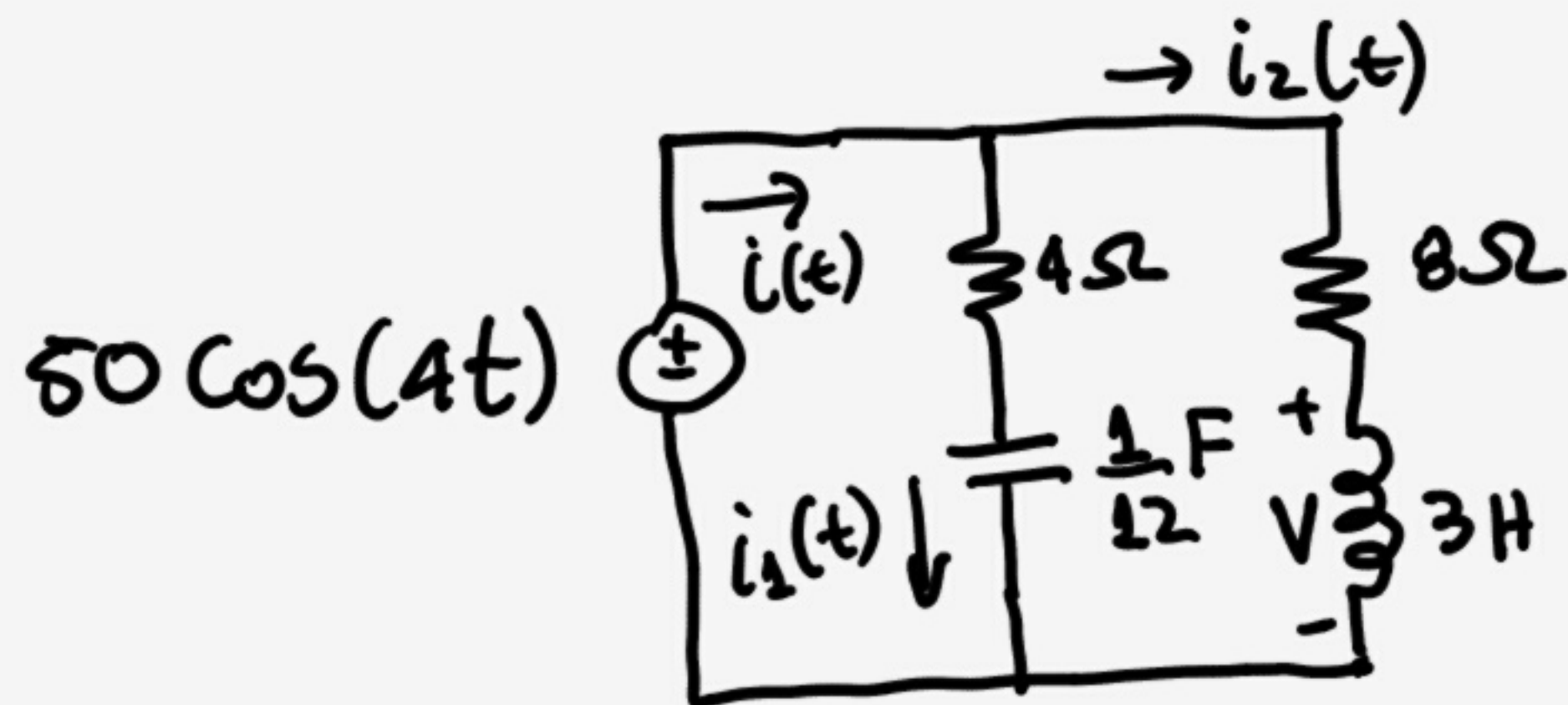


5) Hallar $i(t)$.

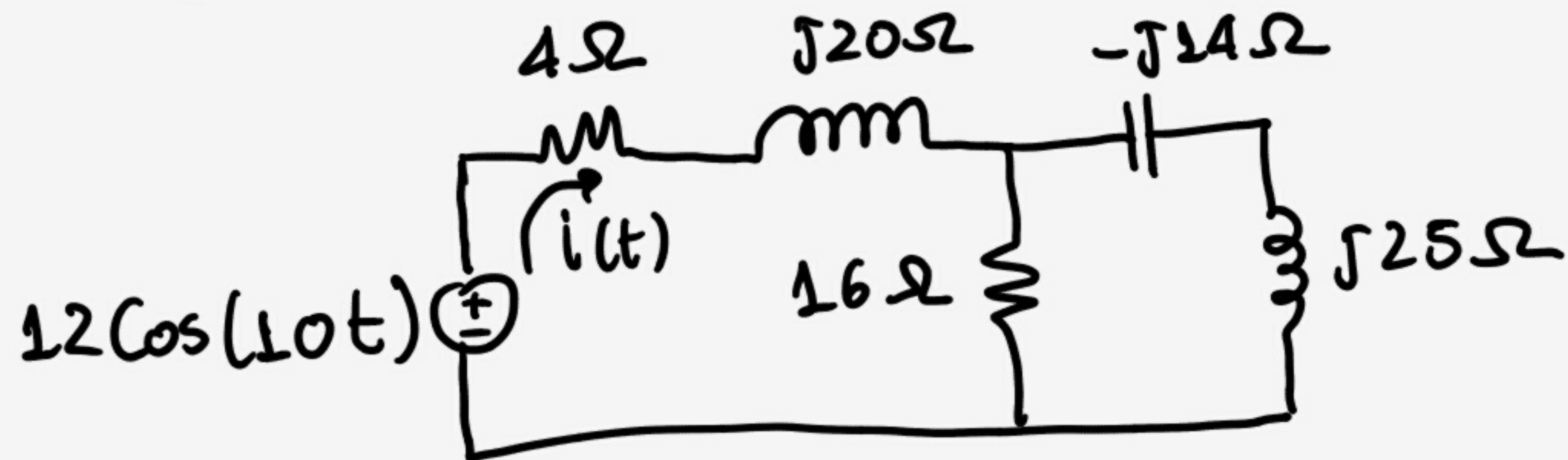


6) Hallar $v(t)$.

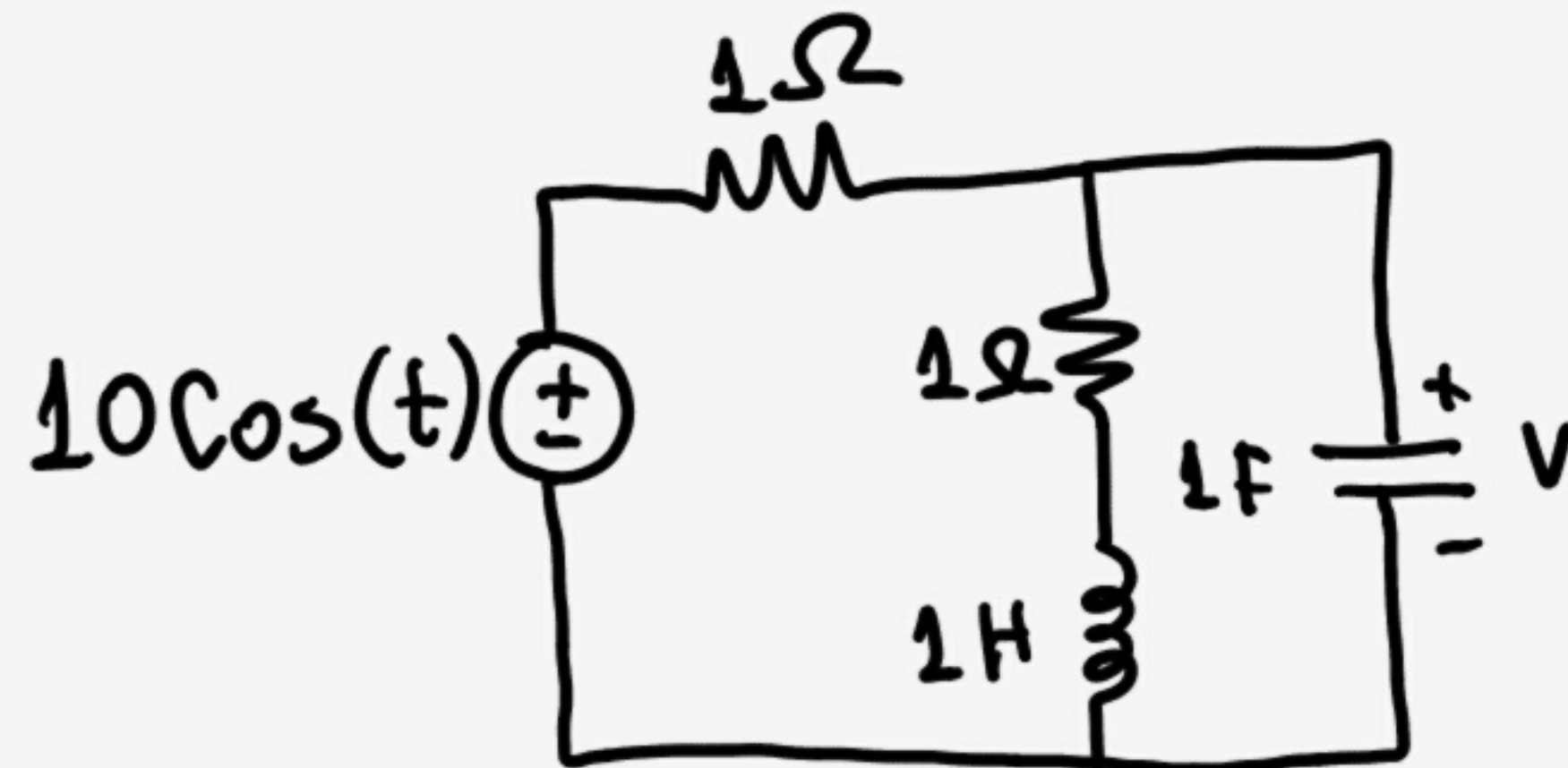

7) Calcule $v_o(t)$.

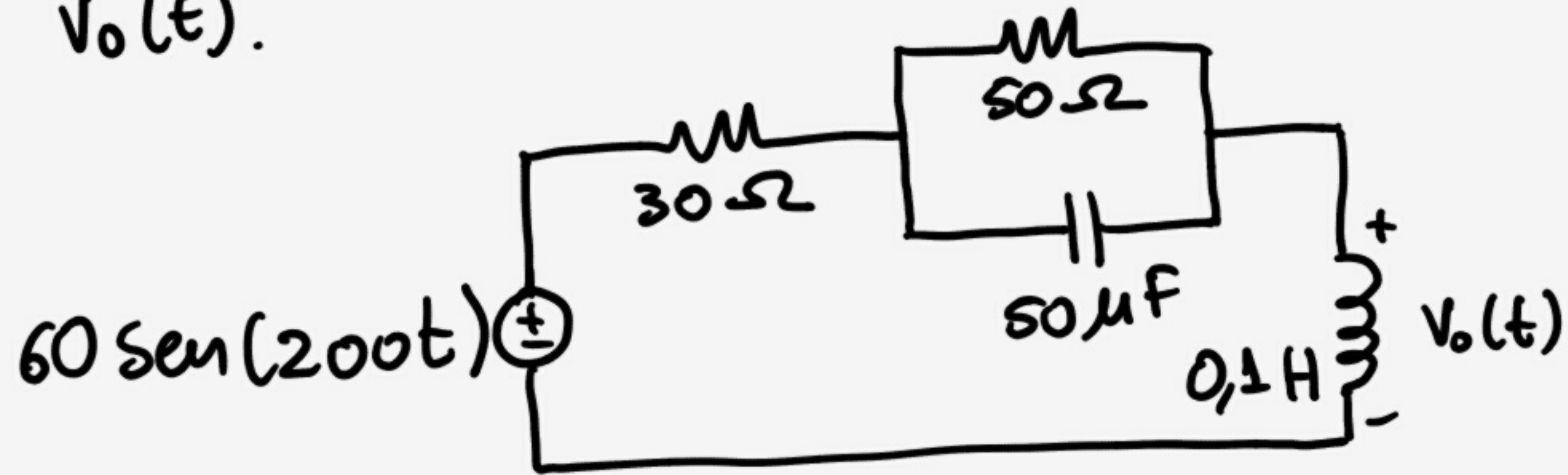


8) Halle $i_o(t)$.

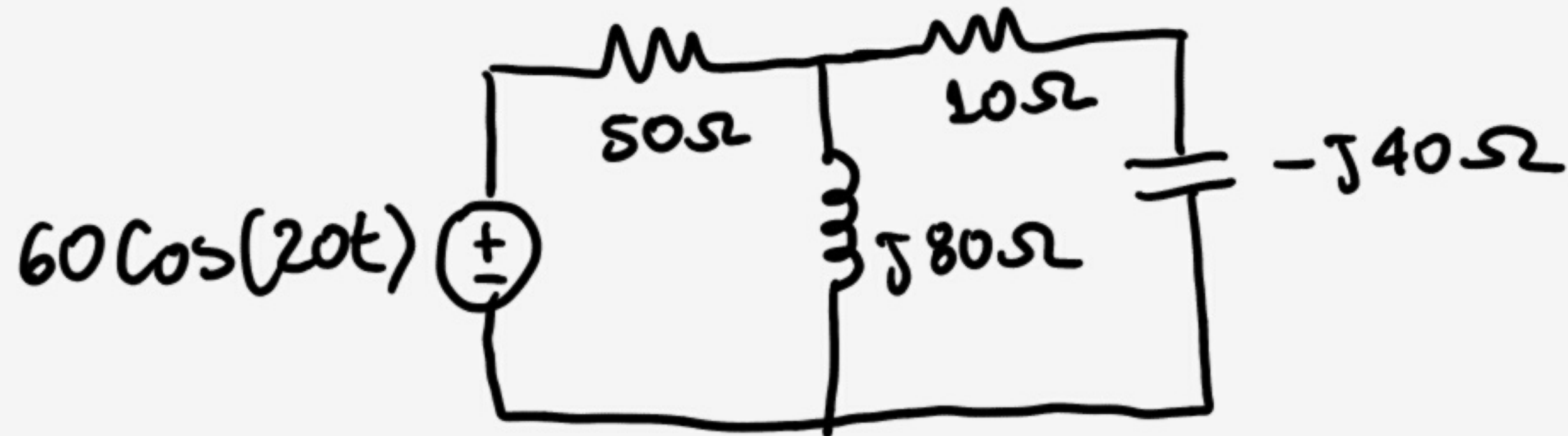


9) Calculate $i(t)$:


a)

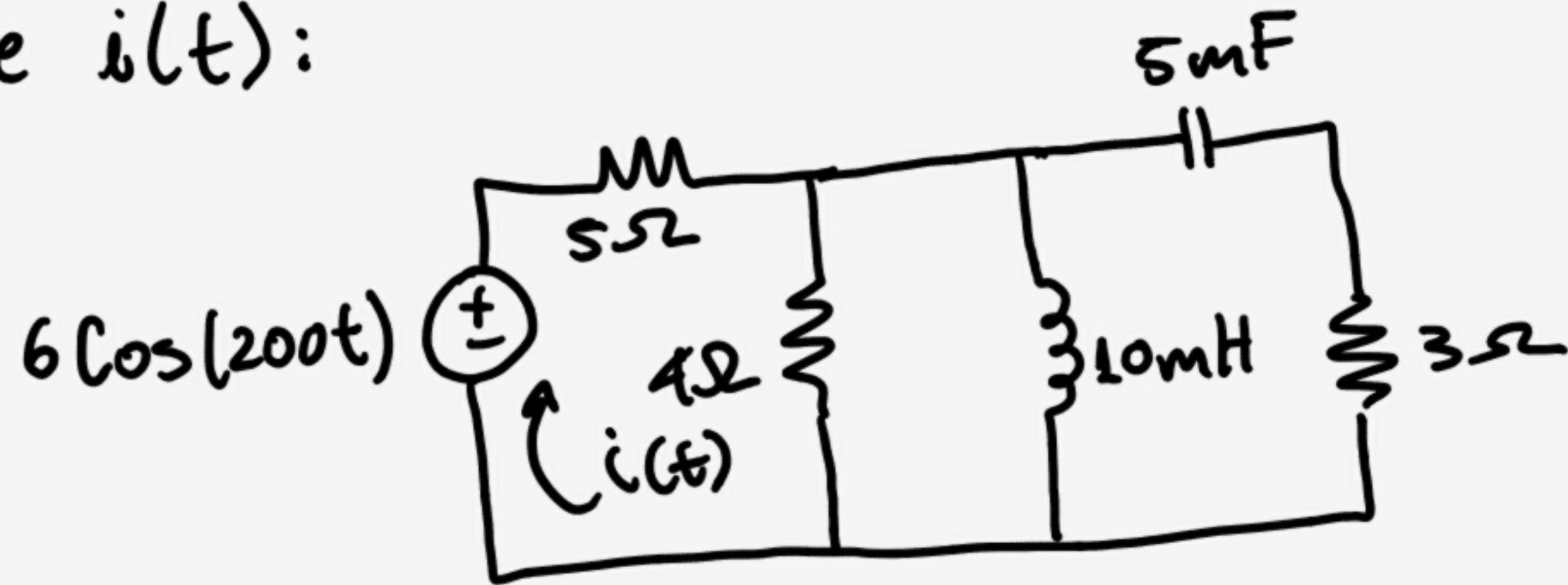

b)

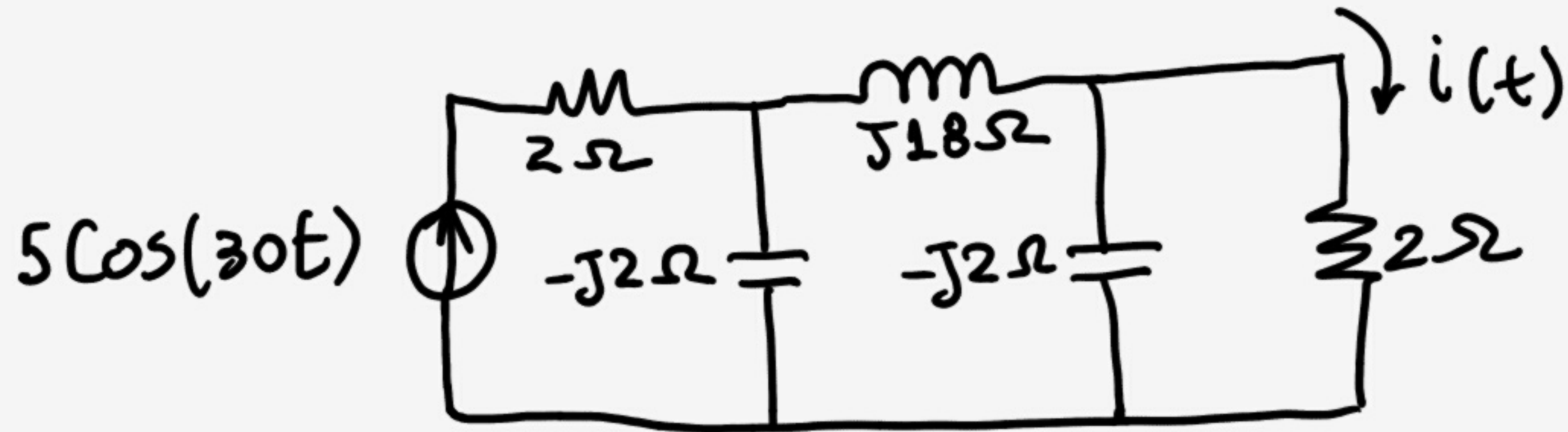

10. Halle i_x :

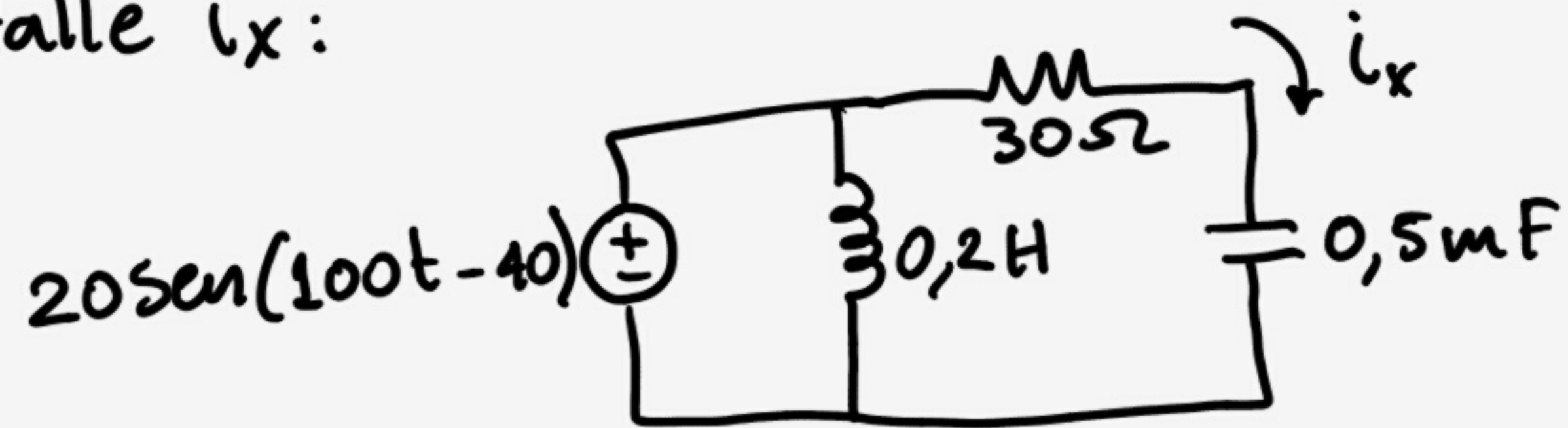

11. Halle v_x .

